

# **Arduino Theremin**

Written By: Alan



- Hot Glue gun & hot glue (1)
- Soldering iron (1)
- Super glue (1)

## PARTS:

- Arduino microcontroller, Uno or Duemilanove (1)
- Breadboard kit (1)
- 3-16V Piezo Buzzer (RadioShack #273-074) (1)
- VEX Ultrasonic Range Finder (1)
- CdS Photoresistor (1)
- 10K Resistor (1)
- Potentiometer, 5kΩ, audio taper (1)
- Servo (generic) (1)
- Circuit board header: 3-pin (1)
- Breadboard jumper wires, or solid core
  22AWG wire (Many)
  Many colours
- Wire (A few) Many Colours
- Rubber bands (A few)
- Dowel, 3/8" dia. 1/2" length (1)
  Or near
- Sandpaper (1)
  Strip, 1/2" x 2"


#### **SUMMARY**

If you want to make music, then this project is for you. This is a theremin-like device to

control the pitch and volume of a musical note. It utilizes a photo-resistor to control the pitch, and an ultrasonic sensor to control a servo which turns a potentiometer controlling the volume.

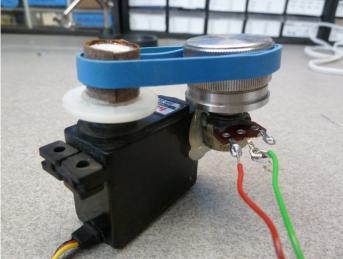
### **Step 1** — Connect the servo and potentiometer.







- Solder wires onto the potentiometer. I used red for the audio voltage in on the left and green for the voltage out in the center.
- I initially soldered on a black wire on the third pin, but removed it as it was redundant.
- Hot glue the dowel onto the servo, centered, and then super glue the sandpaper to the dowel to provide traction for the rubber band.
- Find a rubber band, preferably wide, that can be used to transfer the servo motion to the potentiometer.
- Hot glue the potentiometer in place. Don't be sparing with the hot glue, as it is not terribly strong.
- Turn both the potentiometer and servo all the way to the left and link them together with the rubber band. I had to use several as the servo shifted while the glue was cooling.

#### **Step 2** — Wire that Arduino.

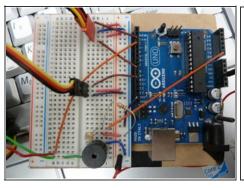

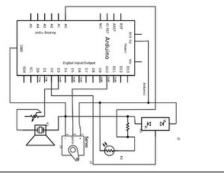

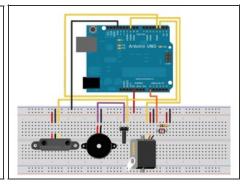

- Supply +5V to the power rail on the breadboard, and then to the power pin on each ultrasonic sensor, the servo power pin, and the photo-resistor.
- Supply GND to the GND rail on the breadboard, and then to the ground pin on each ultrasonic sensor, the servo ground pin, and the piezo buzzer ground pin.
- I used analog 0 for the photo-resistor output, digital 10 for the servo, digital 2 for the ultrasonic output, and digital 8 for the ultrasonic input
- Use a 10kΩ resistor as a pull-down for the photo-resistor by connecting it to GND and analog 0, or whatever analog pin you end up connecting the photo-resistor to.

### **Step 3** — Code the Arduino.



- See attached file, theremin.pdf, for the code.
- The volume should increase as your hand is moved closer to the ultrasonic sensor, so if the opposite happens, simply reverse the mapping of the servo position.
- To do this, change the code from rad = map(dist, 8, 20, 0, 90); to rad = map(dist, 8, 20, 90, 0);

This document was last generated on 2013-02-14 01:46:07 AM.